

Basic Electronics Part 4
by
Thomas Atchison W5TV

Recall that if we have a string of resistors, R_1 , R_2 , R_3 , in series, we can find a single equivalent resistor, R_T , to replace that string using the formula

$$R_T = R_1 + R_2 + R_3.$$

Similarly, if we have a string of resistors, R_1 , R_2 , R_3 , in parallel, we can find a single equivalent resistor, R_T , to replace that string using the formula

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}.$$

We now consider how to use these equivalent relationships to simplify a series/parallel circuit. Consider figure 1

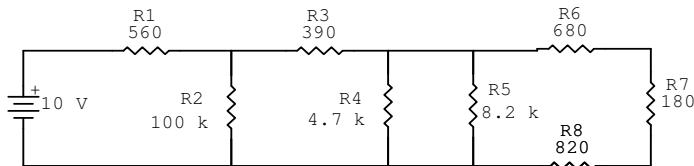


Fig. 1

We begin working at the point farthest from the voltage source. Notice that resistors R_6 , R_7 , and R_8 are in series. This means we can replace them with one equivalent resistor, $R_9 = R_6 + R_7 + R_8$. The value of R_9 is 1680 ohms. This leaves us with the equivalent circuit in figure 2

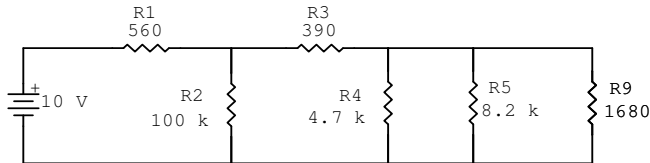


Fig. 2

In figure 2 we observe that the three resistors, R_4 , R_5 , and R_9 , are connected in parallel. This means we can replace them with one equivalent resistor, R_{10} as follows:

$$\frac{1}{R_{10}} = \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_9}.$$

The value of R_{10} is 1075 ohms. This leaves us with the equivalent circuit in figure 3

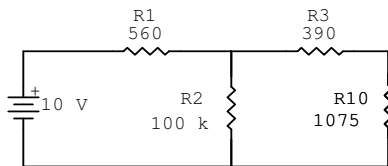


Fig. 3

In figure 3, R_3 and R_{10} are in series, so we can replace them with an equivalent resistor, R_{11} having a value of 1465 ohms. This leads to the equivalent circuit in figure 4

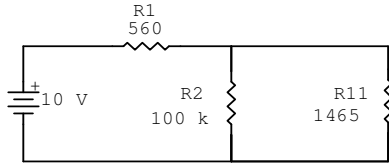


Fig 4

Now we see that R2 and R11 are in parallel so we can replace them with an equivalent resistor, R12, having a value of 1444 ohms. This leads to the circuit in figure 5

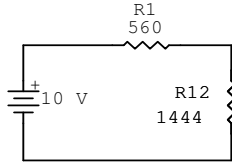


Fig 5

This is a series circuit and we can now write a final equivalent circuit shown in figure 6



Fig 6

We may now calculate the total current that flows from the voltage supply using this equivalent resistor. Ohm's Law is used as follows:

$$I = \frac{E}{R_{13}} = \frac{10}{2004} = 4.99 \times 10^{-3}$$

The total current is 4.99 mA.