

Basic Electronics Part 27  
by  
Thomas Atchison W5TV

We return to a circuit with resistance, R, inductance L, and an alternating voltage source. (Fig. 1)

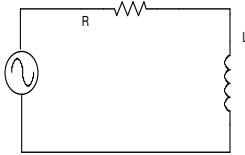


Fig. 1

Since this is a series circuit, the same current,  $I$ , flows through both R and L. Each component has its own series voltage drop. For the resistor, R, the voltage drop is  $I R$ . If the inductor has inductive reactance  $X_L$  then the voltage drop across the inductance is  $I X_L$ .

Now, suppose  $R=100\Omega$  and we measure the current as  $I=1$  amp. Then the voltage drop across R is  $V_R=I R$  so  $V_R=100$  volts. Similarly, if the inductive reactance is  $X_L=100\Omega$ , then the voltage drop across L is  $V_L=I X_L$ . This means that  $V_L=100$  volts. Following the same procedure as in Basic Electronics, Part 26, the total voltage,  $V_T$ , will be

$$\begin{aligned} V_T &= \sqrt{(I R)^2 + (I X_L)^2} \\ &= \sqrt{100^2 + 100^2} \\ &= \sqrt{20000} \\ &= 141 \text{ volts.} \end{aligned}$$

The total opposition to current in a circuit is called the impedance. Impedance is denoted by  $Z$ . The relation connecting the impedance to the current and the total voltage is

$$V_T = I Z.$$

In this case,  $V_T=141$  volts and  $I=1$  amp, so  $Z=141\Omega$ .

Using the above equation for  $V_T$ , we have

$$I Z = \sqrt{(I R)^2 + (I X_L)^2}.$$

This leads to

$$I Z = I \sqrt{R^2 + X_L^2}.$$

We can divide out the common I to get

$$Z = \sqrt{R^2 + X_L^2}.$$

Let's consider an example. Suppose we have  $R=30\Omega$  and  $X_L=40\Omega$  in a series circuit with an alternating voltage of 100 volts applied. In this case the circuit impedance,  $Z$ , is

$$Z = \sqrt{900 + 1600}.$$

So  $Z=50\Omega$ .

The current,  $I$ , is given by

$$I = \frac{V_T}{Z}$$

so we have  $I=100/50=2$  amps.

The voltage across the resistor is given by

$$V_R = (2)(30) = 60 \text{ volts,}$$

and the voltage across the inductance is given by

$$V_L = (2)(40) = 80 \text{ volts.}$$

The phase angle can be calculated using the reactance and the resistance as follows:

$$\tan \theta = \frac{X_L}{R}.$$

Here  $\tan \theta = 40/30 = 1.333$  so we have  $\theta = 53^\circ$ . This means that  $I$  lags  $V_T$  by  $53^\circ$ .

Note that

$$\begin{aligned} V_T &= \sqrt{V_R^2 + V_L^2} \\ &= \sqrt{60^2 + 80^2} \\ &= \sqrt{3600 + 6400} \\ &= \sqrt{10000} \\ &= 100 \text{ volts.} \end{aligned}$$